

1. Design a Single cell - 1 bit Carry Propagate (Ripple Carry Adder) full adder.

a. Generate the truth table

A	B	C <sub>in</sub>	Sum	C <sub>out</sub>
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

b. Using K-map, determine the logical expression for Carry out (C-out) and Sum (S)

Sum

	BC	00	01	11	10
A	0		1		1
	1	1		1	

$$\begin{aligned}
 \text{Sum} &= \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + A\bar{B}\bar{C} + A\bar{B}C \\
 &= A(\bar{B}\bar{C} + BC) + \bar{A}(\bar{B}C + B\bar{C}) \\
 &= A(\overline{B \oplus C}) + \bar{A}(B \oplus C)
 \end{aligned}$$


$$\text{Sum} = A \oplus B \oplus C_{in}$$

Cout

	BC	00	01	11	10
A	0			1	
	1		1	1	1

$$\text{Cout} = AC_{in} + AB + BC_{in}$$

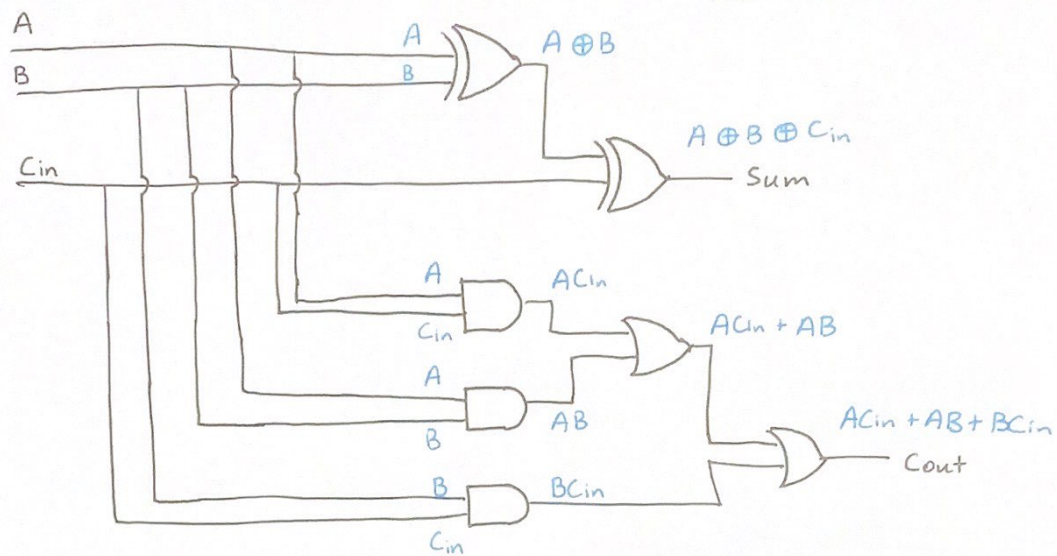C. Based on the logical expression, create the schematic diagram for full adder.





2. Design a 1 bit, 2 to 1 multiplexer (Mux). Outputs Y when  $S=0$ ; X when  $S=1$ .

a. Generate the truth table.

S	$I_1$	$I_0$	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

b. Using K-map, determine the logical expression for output.

Y S	$I_1 I_0$			
	00	01	11	10
0		1	1	
1			1	1

$$Y = \bar{S}I_0 + SI_1$$

c. Based on the logical expression, create the schematic diagram for Mux.

