

Problem I: Consider the sequential circuit in Figure 5.31 where the adder is a CLA. Its simplified circuit is shown in Figure 5.32. Assuming that the Flip-Flops register set-up time, clock-to-q, and clock-skew are each 0.1 ns, determine the upper bound for its clock frequency. (4 pts)

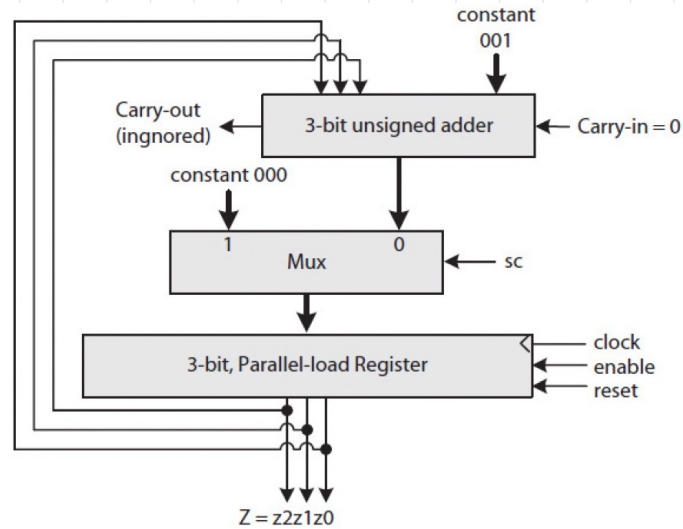


FIGURE 5.31 A synchronously cleared bit-parallel mod-8 up-counter.

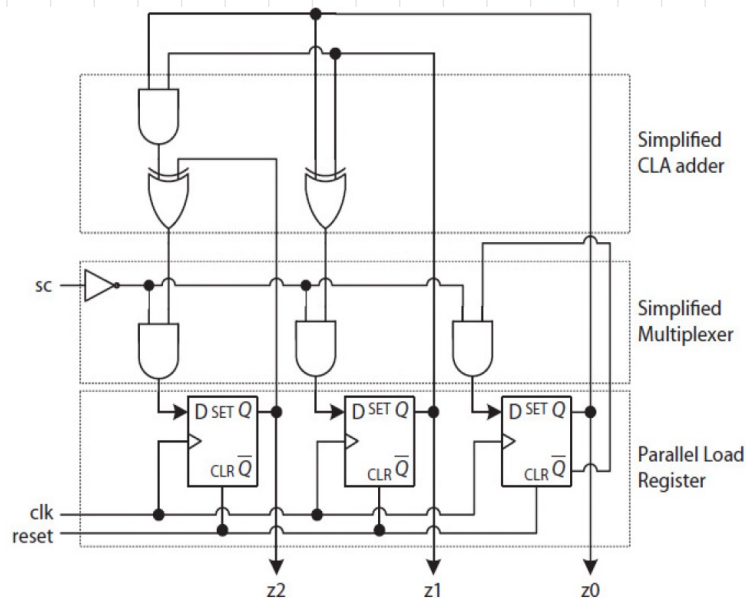


FIGURE 5.32 A synchronously cleared bit-parallel mod-8 up-counter using a simplified CLA adder and a simplified MUX.

The longest path delay for the simplified circuit is:


$$\Delta_{AND} + \Delta_{XOR} + \Delta_{AND} = 0.2 + 0.3 + 0.2 = 0.7 \text{ ns}$$

$$T \geq 0.7 + 3(0.1) = 1.0 \text{ ns}$$

$$F \leq 1 \text{ GHz}$$

Problem II: Textbook problem 5.9 assuming the unknown state are ignored (don't care) in the design. (5 pts)

 5.9. Design a Mealy sequence recognizer that detects the nonoverlapping sequence "101." Use binary encoded state labels and draw the circuit schematic similar to the one shown in Fig. 5.16.




Number of bits =  $\log_2[k]$ , where  $k = \#$  of states

$$\log_2(3) = 2$$


Current State		Input	Next State		Output
$q_1$	$q_0$	$x$	$d_1$	$d_0$	$z$
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	1	0	0
0	1	1	0	1	0
1	0	0	0	0	0
1	0	1	0	0	1
1	1	0	x	x	x
1	1	1	x	x	x

$$d_1 = \bar{q}_1 q_0 \bar{x} \quad d_0 = \bar{q}_1 \bar{q}_0 x + \bar{q}_1 q_0 x$$


$$z = q_1 \bar{q}_0 x$$

 


$$d_1 = q_0 \bar{x}$$

 

$$d_0 = \bar{q}_1 x$$

 

$$z = q_1 x$$

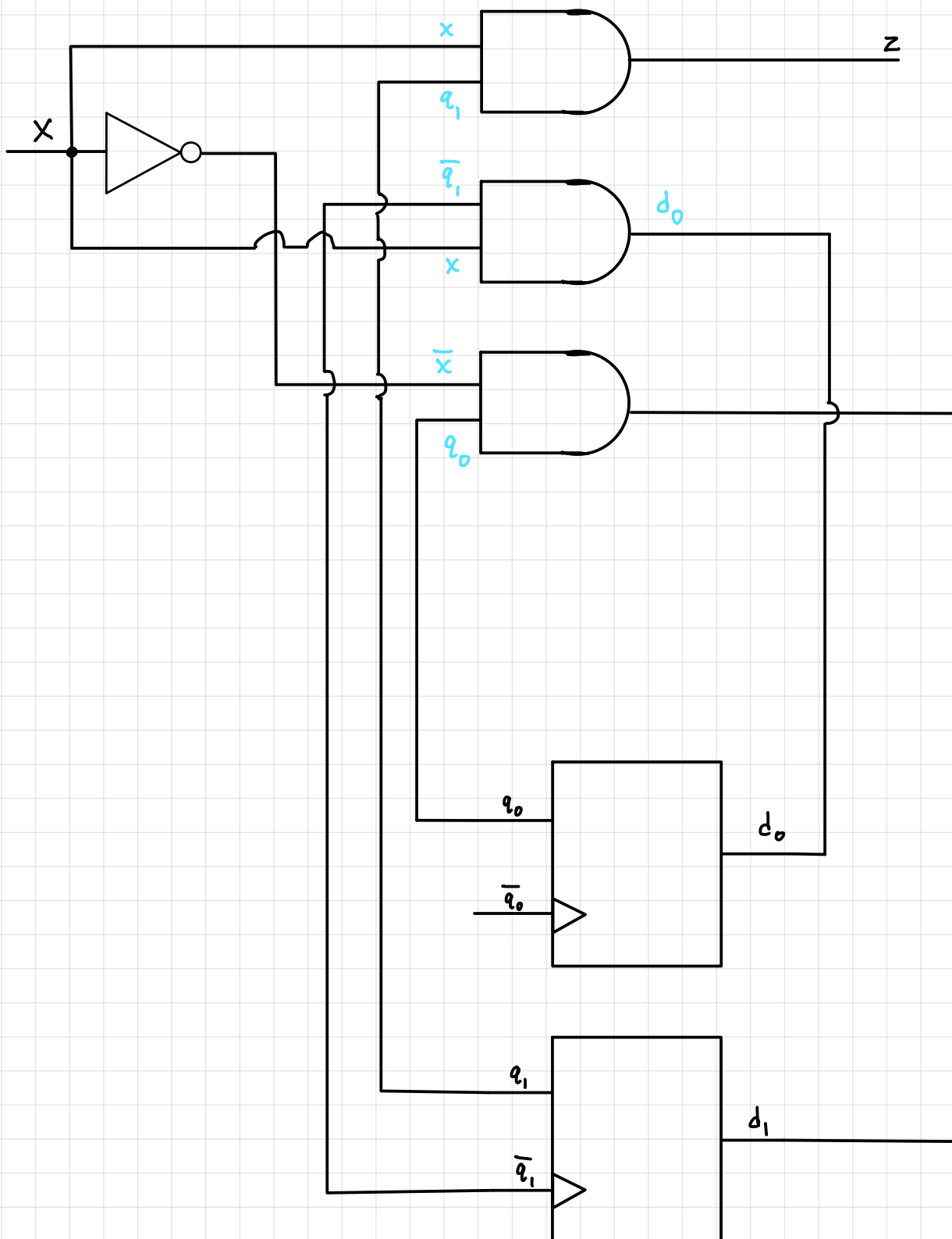

Problem III: Textbook problem 5.11 (only FSD) (3 pts)

5.11. Design a Mealy sequence recognizer that detects the overlapping sequence "1001." Use binary encoded state labels.

